

# EE309: IITB-RISC

Akshay Kaushal Raushan Kumar Monu Kumar Yadav


May 7, 2022

## 1 DATAPATH

The method of designing the final datapath is as follows:

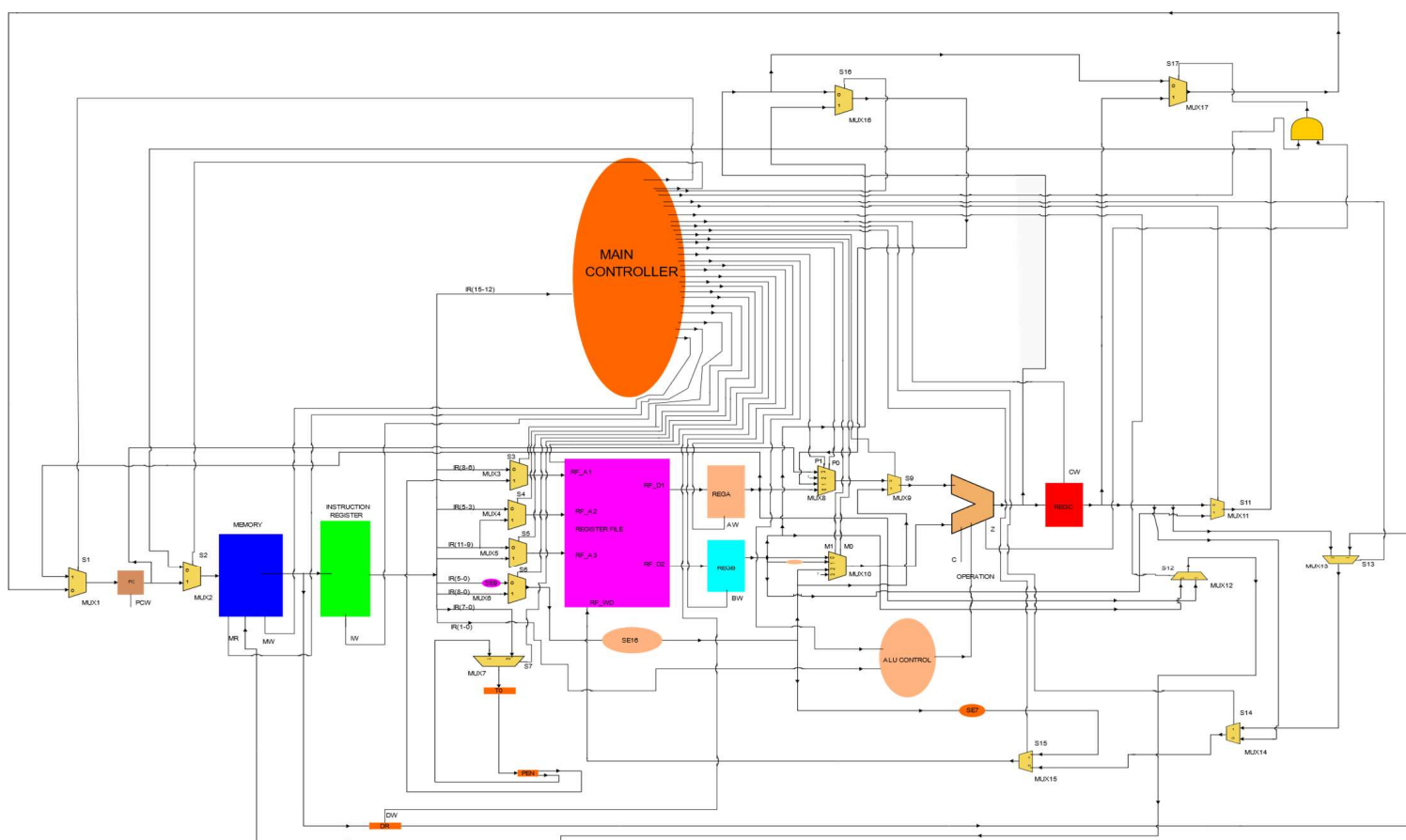1. First we divided the instructions into their respective category of R,I and J
2. Started with R type instructions to make the datapath for each instruction separately and then combining it to get the final datapath for R type instruction.
3. We designed datapath of one instruction at a time and then added the design of next instructions by improvising the existing design.

Below is the descriptive datapath with controller (both ALU and MAIN controller) designed using **Inkspace** software showing all the labels appropriately.




# FLOWCHART


RAUSHAN KUMAR  
MONU KUMAR YADAV  
Akshay Kaushal

R-Type instruction

Op_code	Rc	Rb	a	c	fn
15 – 12	11–9	8–6	5–3	2	1–0

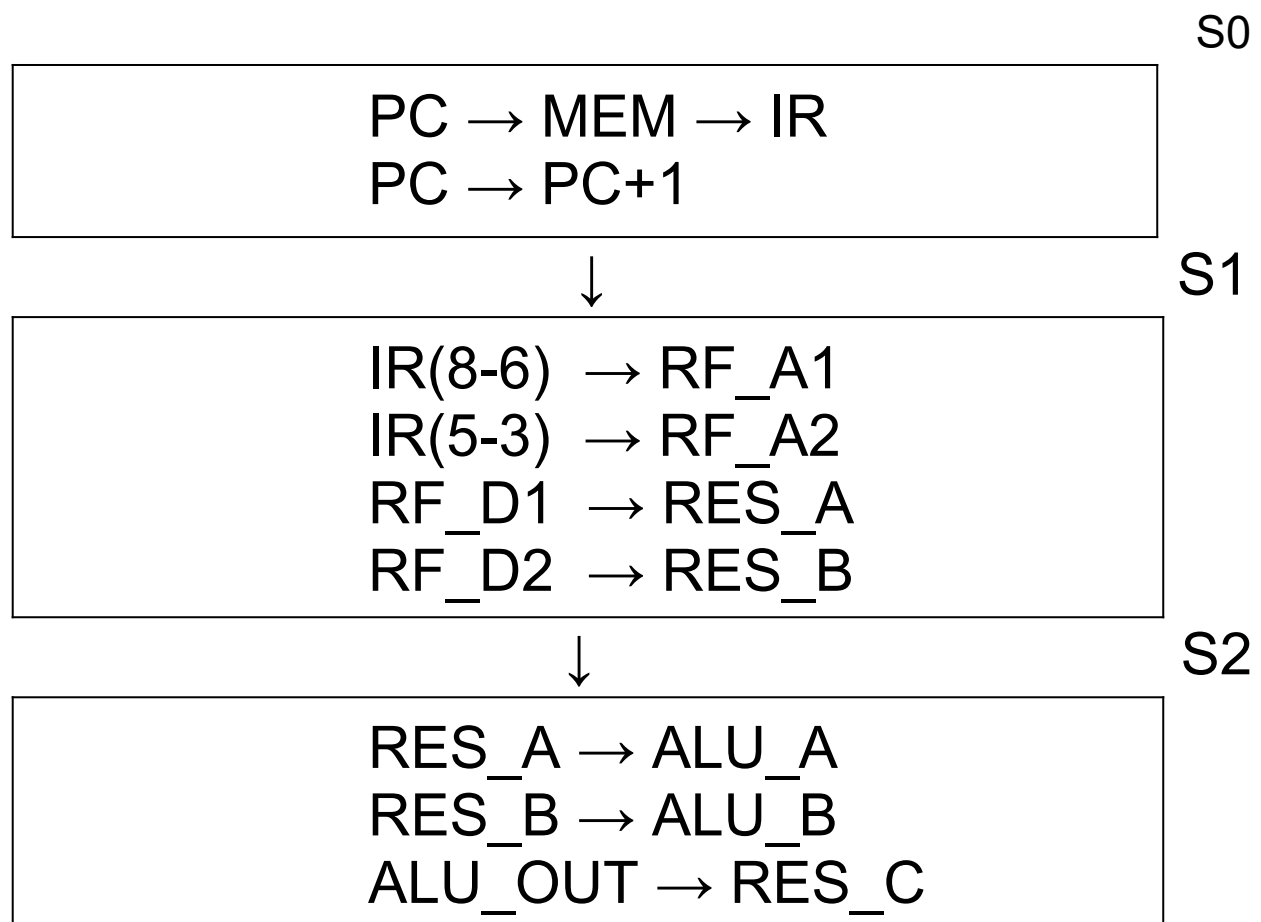

S3

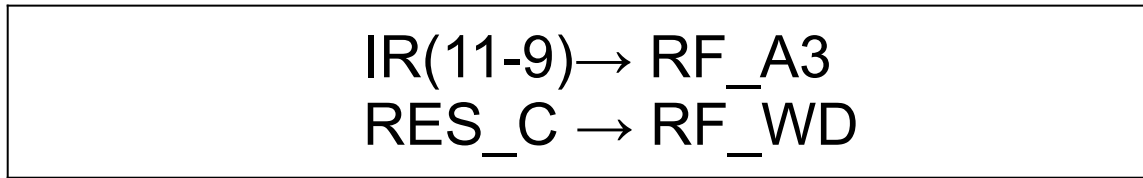


I-Type instruction


ADI:-

Op_code	Rb	Ra	IMM-6BIT
15 – 12	11 – 9	8 – 6	5 — 0


S0

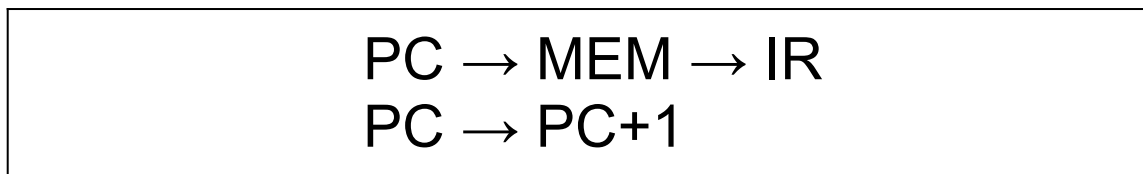


S4

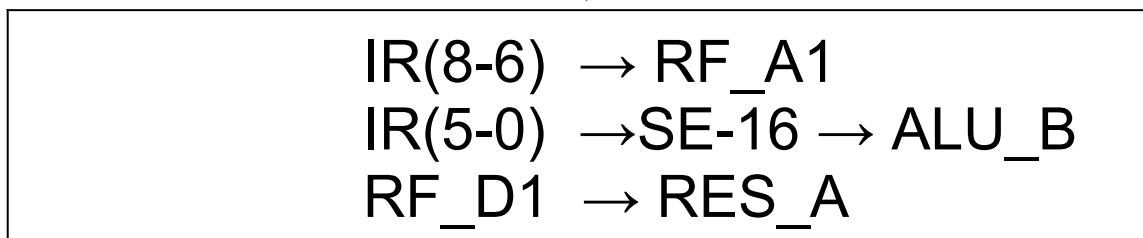

S5

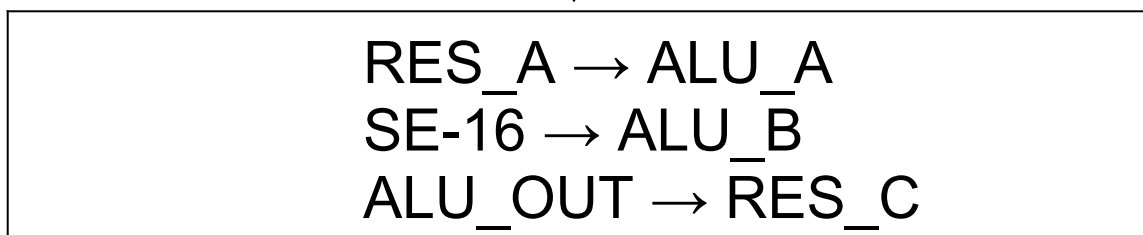


S3

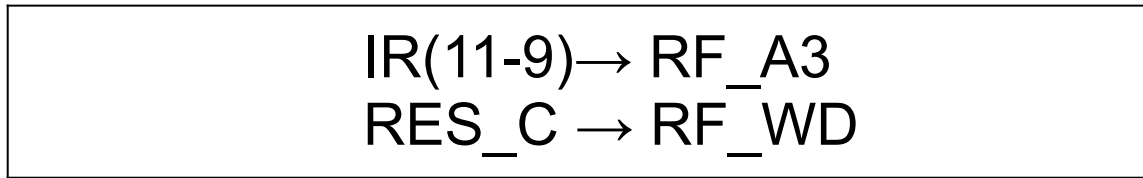


LW:-

Op_code	Rb	Ra	IMM-6BIT
15 – 12	11 – 9	8 – 6	5 — 0


S0

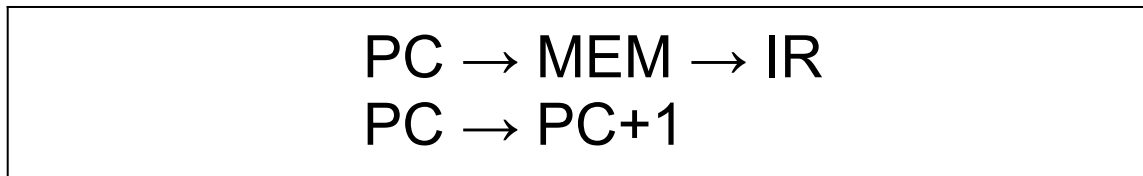

S4

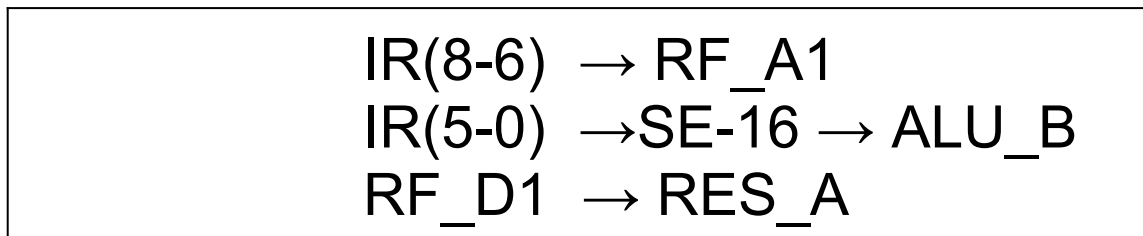

S5

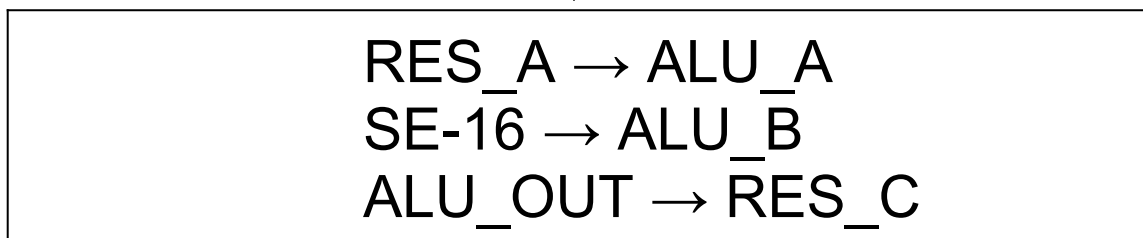

S6

RES\_C  $\rightarrow$  ADDR<sub>M</sub>  
 RD  $\rightarrow$  DR  $\rightarrow$  RF\_WD  
 IR(11-9)  $\rightarrow$  RF\_A3

SW:-

Op_code	Rb	Ra	IMM-6BIT
15 – 12	11 – 9	8 – 6	5 — 0

S0

PC  $\rightarrow$  MEM  $\rightarrow$  IR  
 PC  $\rightarrow$  PC+1



S4

IR(8-6)  $\rightarrow$  RF\_A1  
 IR(5-0)  $\rightarrow$  SE-16  $\rightarrow$  ALU\_B  
 RF\_D1  $\rightarrow$  RES\_A



S5

RES\_A  $\rightarrow$  ALU\_A  
 SE-16  $\rightarrow$  ALU\_B  
 ALU\_OUT  $\rightarrow$  RES\_C



S7

$RES\_C \rightarrow ADDR\_M$   
 $IR(11-9) \rightarrow RF\_A2$   
 $RF\_D2 \rightarrow RES\_B$   
 $RES\_B \rightarrow WD$

BEQ:-

Op_code	Rb	Ra	IMM-6BIT
15 – 12	11 – 9	8 – 6	5 — 0

S0

$PC \rightarrow MEM \rightarrow IR$   
 $PC \rightarrow PC+1$



S8

$IR(11-9) \rightarrow RF\_A2$   
 $IR(8-6) \rightarrow RF\_A1$   
 $RF\_D1 \rightarrow RES\_A \rightarrow ALU\_A$   
 $RF\_D2 \rightarrow RES\_B \rightarrow ALU\_B$



S9

$IR(5-0) \rightarrow SE-16 \rightarrow ALU\_B$   
 $PC \rightarrow ALU\_A$   
 $ALU\_OUT \rightarrow RES\_C$

S10



IF(A==B){  
RES\_C → PC}

JLR:-

Op\_code

Ra

Rb

IMM-6BIT

15 – 12

11 – 9

8 – 6

000000

S0

PC → MEM → IR  
PC → PC+1



S11

PC → ALU\_A  
+1 → ALU\_B  
IR(11-9) → RF\_A3  
ALU\_OUT → RF\_WD



S12


IR(8-6) → RF\_A1  
RF\_D1 → RES\_A → PC



## J-Type instruction:-

LHI:-

Op_code	Ra	IMM-9BIT
15 – 12	11 – 9	8 – 0

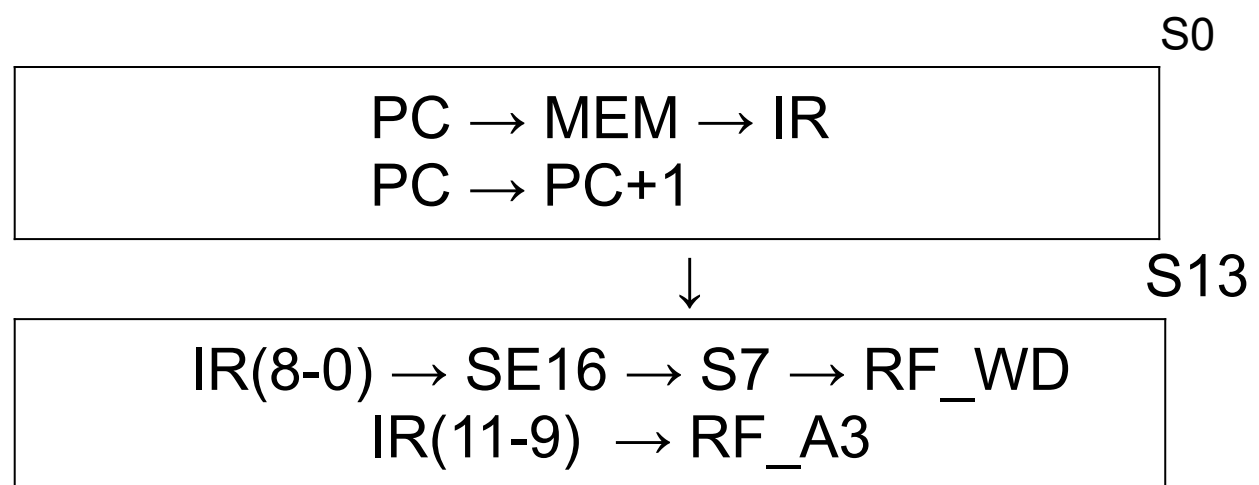

JRI:-


Op\_code

Ra


IMM-9BIT

15 – 12	11 – 9	8 – 0
---------	--------	-------

S0

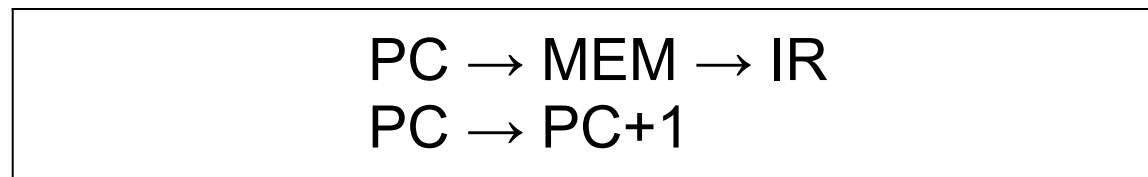

S14

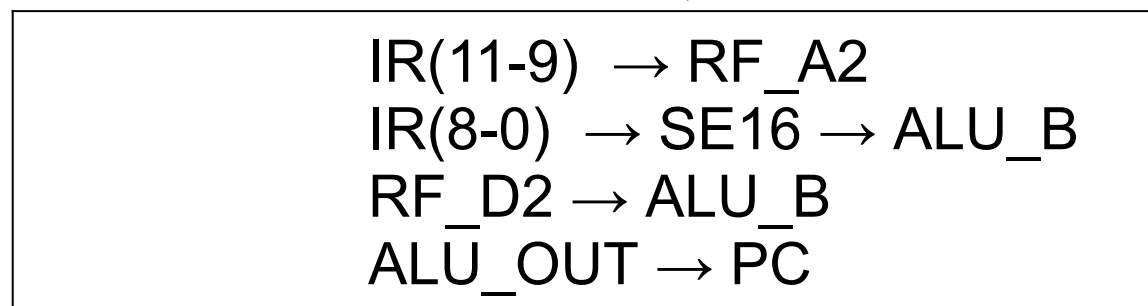

LM:-


Op\_code

Ra


IMM-9BIT

15 – 12	11 – 9	8 – 0
---------	--------	-------

S0

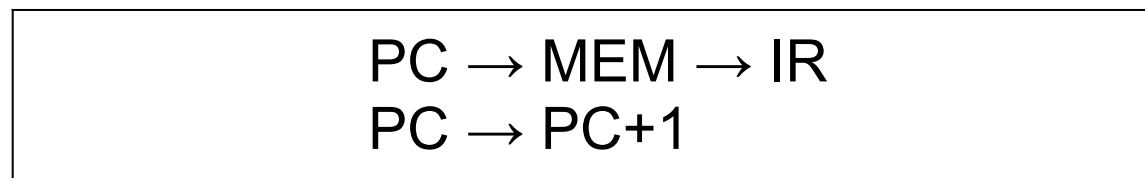

S15

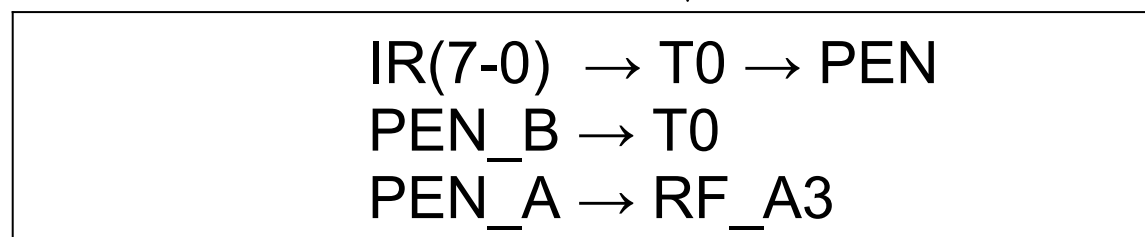

WHILE(PEN\_A!=000)

S16



SM:-


Op\_code

Ra


IMM-9BIT

15 – 12	11 – 9	8 – 0
---------	--------	-------

S0

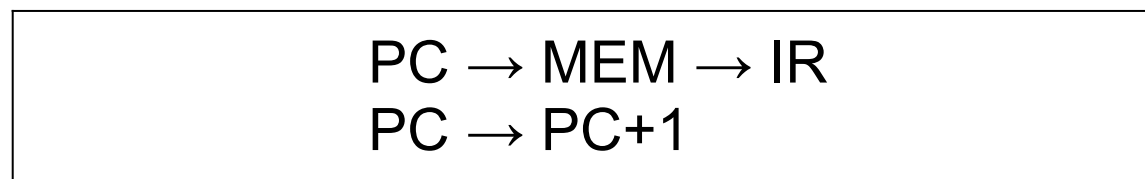


S17

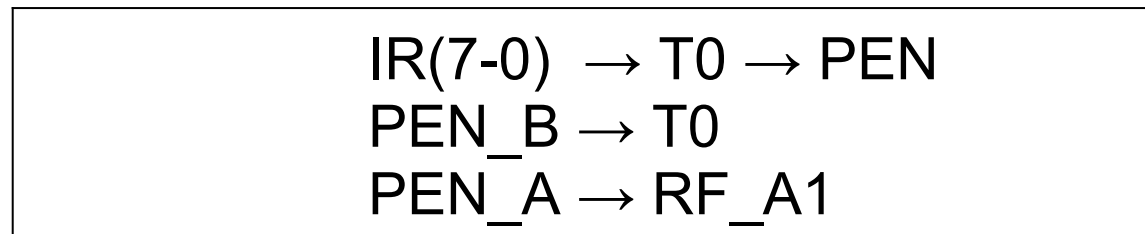

WHILE(PEN\_A!=000)

S18

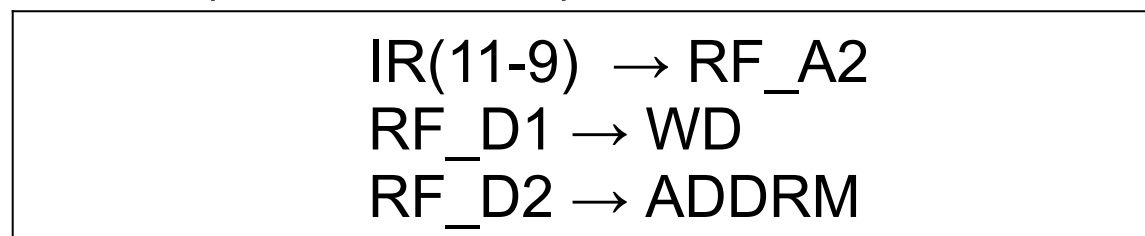

JAL:-


Op\_code

Ra


IMM-9BIT

15 – 12	11 – 9	8 – 0
---------	--------	-------


S0

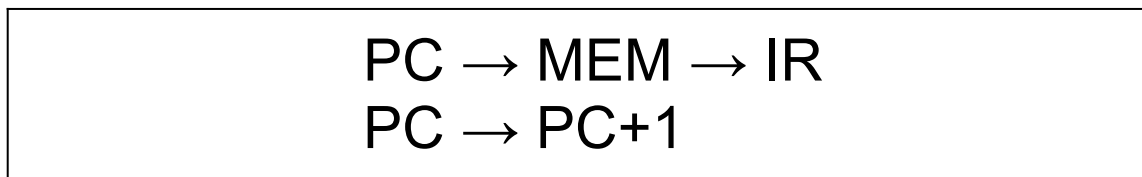

S11

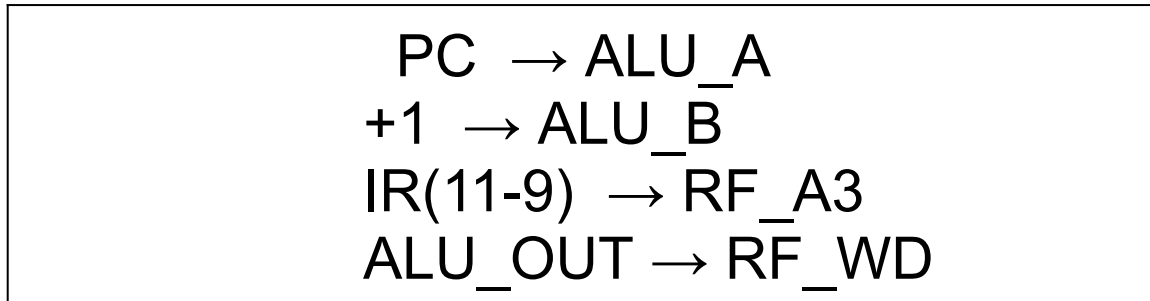

S19

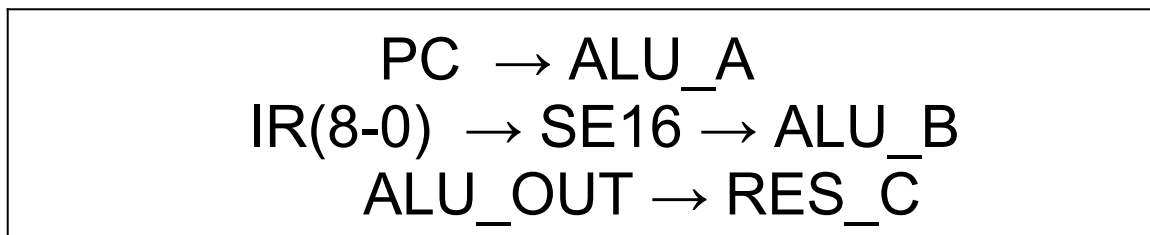

RES\_C → PC

## 2 ALL CONTROL

Our controller takes opcode of 4 bits as an input and gives 28 outputs(27 of 1 bit each and 1 of 2 bits) accordingly make corresponding device ON and OFF for a particular instruction.It decides the following:

1. Whether MUX should be ON or OFF
2. Memory is written or read
3. It sends an output that takes ALU controller as an input to decide which type of instruction it is like R,I or J type of instruction.
4. Whether ALU operation will take place or not

Basically it is the component of hardware design that decides what to do according to opcode.

We made a table to see which device is ON or OFF for an instruction and then got an minimised expression by solving the respective K-map.All the truth table and corresponding minimized boolean expressions are given at the end of the report all in one.

INSTRUCTION	OPCODE INPUT	MUX_1	MUX_2	MUX_3	MUX_4	MUX_5	MUX_6	MUX_7	MUX_8		MUX_9	MUX_10		MUX_11	MUX_12	MUX_13	MUX_14	MUX_15	MUX_16	MUX_17	MEM		IR	DR	RF	ReA	ReB	ReC
									P1	P0		M1	M0								S11	S12						
ADD	R-TYPE	0001	0	0	0	0	X	X	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
ADC	R-TYPE	0001	0	0	0	0	X	X	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
ADZ	R-TYPE	0001	0	0	0	0	X	X	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
ADL	R-TYPE	0001	0	0	0	0	X	X	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
NDU	R-TYPE	0010	0	0	0	0	X	X	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
NDC	R-TYPE	0010	0	0	0	0	X	X	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
NDZ	R-TYPE	0010	0	0	0	0	X	X	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
ADI	I-TYPE	0000	0	0	X	0	0	X	0	0	1	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
LW	I-TYPE	0111	0	X	0	0	X	0	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
SW	I-TYPE	0101	0	X	0	0	X	0	0	0	0	0	0	X	X	0	1	0	1	1	1	1	1	1	1	1	1	
BEQ	I-TYPE	1000	0	0	1	X	0	X	X	0	X	0	X	X	X	1	0	1	1	1	1	1	1	1	1	1	1	
JLR	I-TYPE	1010	X	0	0	X	0	X	1	X	1	0	0	X	X	1	X	1	1	1	1	1	1	1	1	1	1	
LHI	J-TYPE	0000	0	0	X	0	1	X	X	X	X	X	X	X	X	1	X	1	X	X	X	X	X	X	X	X	X	
LM	J-TYPE	1100	0	X	1	1	X	X	X	X	X	X	X	X	1	X	1	0	X	X	X	1	1	1	1	1	1	
SM	J-TYPE	1101	0	X	1	X	X	X	X	X	X	X	X	1	1	X	X	X	X	X	X	1	1	1	1	1	1	
JAL	J-TYPE	1001	0	0	X	0	1	X	1	X	1	X	1	X	X	1	X	0	0	X	1	1	1	1	1	1	1	
JRI	J-TYPE	1011	0	0	X	1	1	X	0	0	1	0	0	X	X	1	X	X	X	1	1	1	1	1	1	1	1	



### **3 ALU CONTROLLER**

ALU controller takes 2 input : Function field of 2 bits; and an output of main controller of 2 bits.

Now by taking these 2 as an input, ALU gives an output of 2 bit called operation(addition, subtraction and NAND)

While solving K-map we were facing difficulties with addition and subtraction in the same circuit , that's why we designed ALU keeping addition and subtraction seperately in VHDL.

Truth table and minimized boolean expressions for operations are at the end of the report.


INSTRUCTION		TYPE_BIT		FUNCTION	alu_ctrl
					op
ADD	R-TYPE	00		00	01
ADC	R-TYPE	00		10	01
ADZ	R-TYPE	00		01	01
ADL	R-TYPE	00		11	01
NDU	R-TYPE	00		00	00
NDC	R-TYPE	00		10	00
NDZ	R-TYPE	00		01	00
ADI	I-TYPE	01		XX	01
LW	I-TYPE	01		XX	01
SW	I-TYPE	01		XX	01
BEQ	I-TYPE	01		XX	10
JLR	I-TYPE	01		XX	XX
LHI	J-TYPE	11		XX	XX
LM	J-TYPE	11		XX	01
SM	J-TYPE	11		XX	01
JAL	J-TYPE	11		XX	01
JRI	J-TYPE	11		XX	01
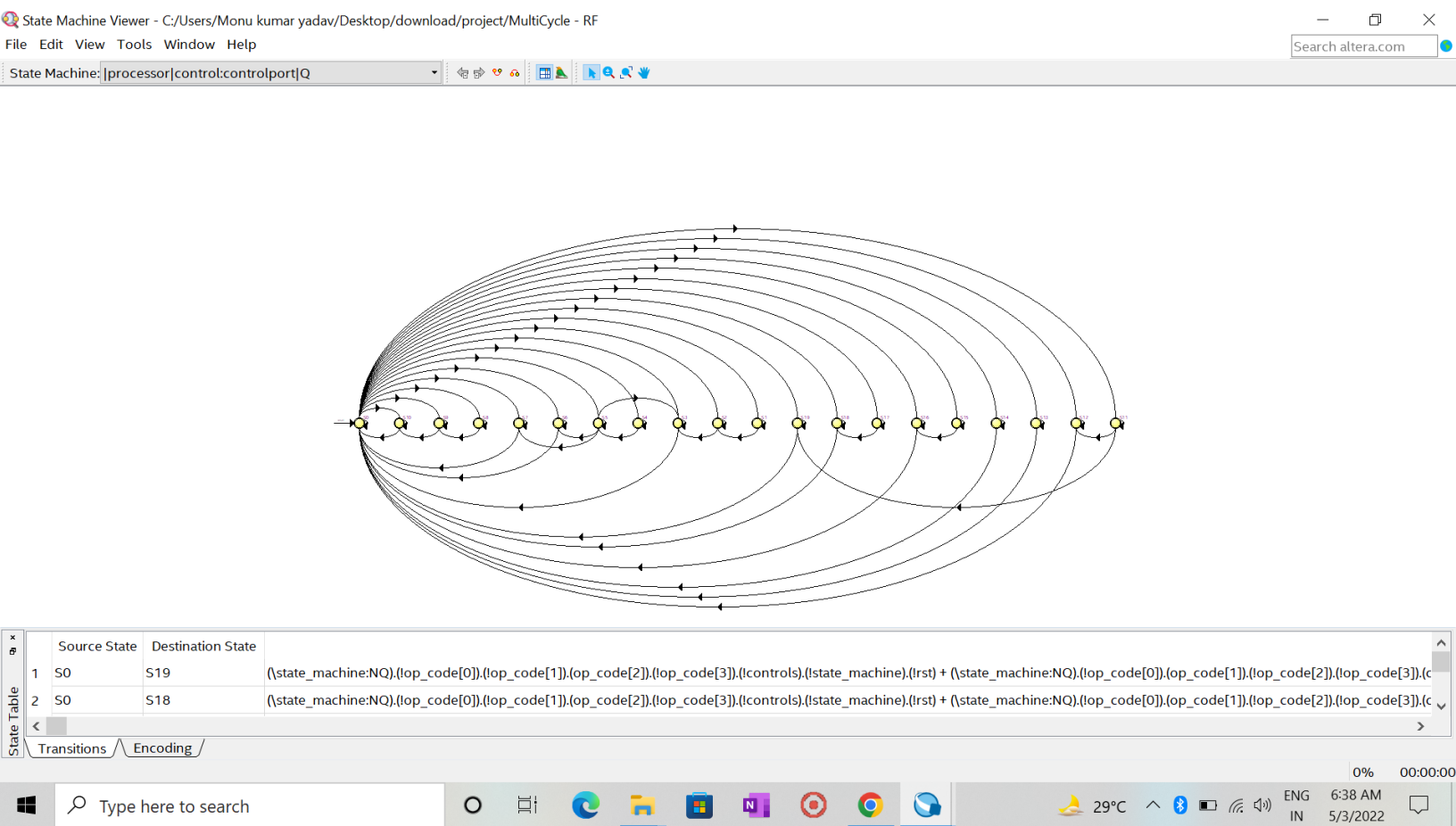
## 4 STATE CONTROLLER

We have used flowchart, opcodes, some additional conditions like C and Z flags to make states and FSM. We also created a table that shows the status of each device based on flowchart.

Truth table and minimized boolean expressions for operations are at the end of the report.





www.32x8.com

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	0	0	0
$\overline{A}.B$	0	1	1	0
$A.\overline{B}$	0	x	0	0
$A.B$	1	x	x	x

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.\overline{B}$	12	13	15	14
$A.B$	8	9	11	10

Groups

(8,9,10,11)	$A.\overline{B}$
(5,7)	$\overline{A}.B.D$

y = AB' + A'BD

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

www.  
32x8  
.com

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$




www.  
32x8  
.com

**Truth Table**

	A	B	C	D	Y
0	0	0	0	0	x
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	x
10	1	0	1	0	x
11	1	0	1	1	x
12	1	1	0	0	0
13	1	1	0	1	x
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022

$$y = AB' + A'BD$$

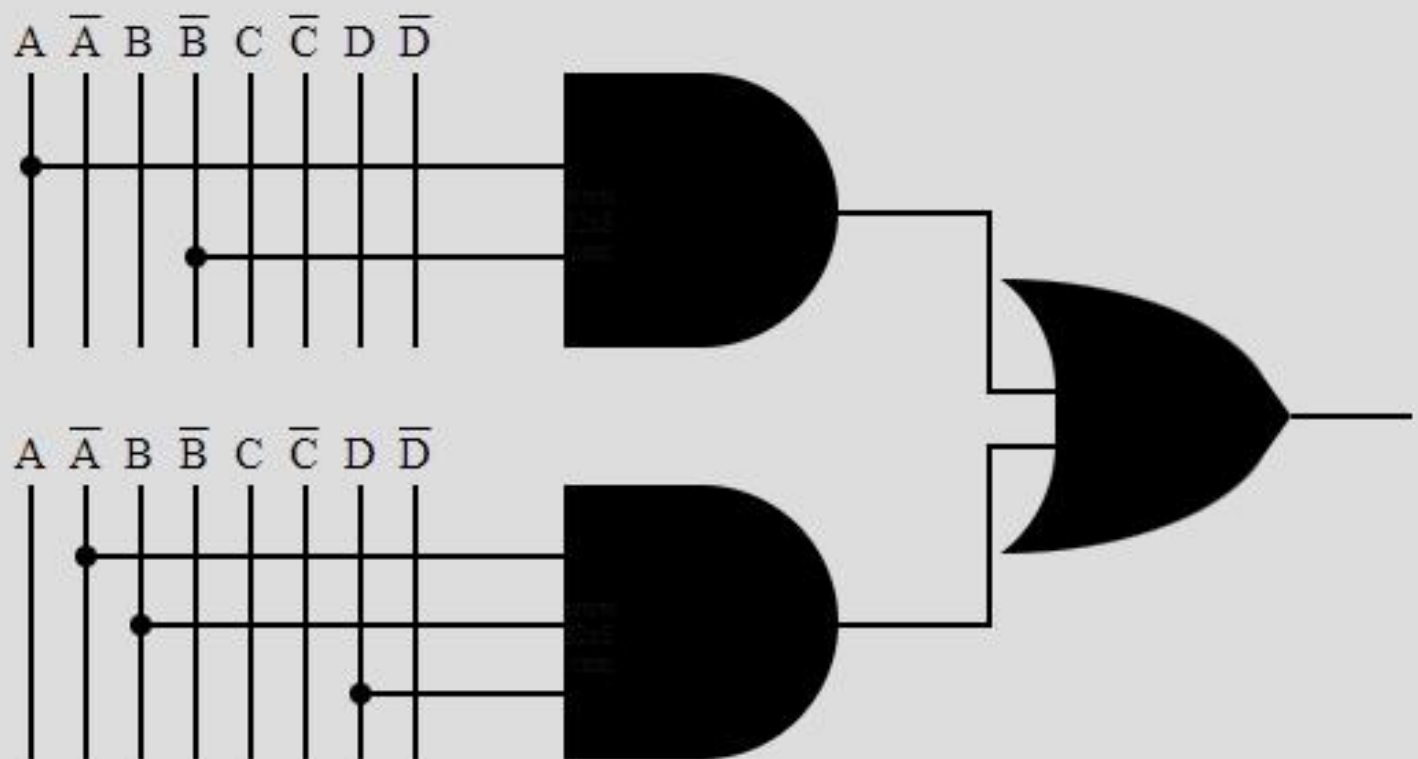



SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	1	1	0	1
$\overline{A}.B$	0	x	x	0
$A.B$	1	1	1	0
$A.\overline{B}$	1	1	1	1

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(0,1,8,9)	$\overline{B}.\overline{C}$
(0,2,8,10)	$\overline{B}.D$
(8,9,12,13)	$A.\overline{C}$
(9,11,13,15)	$A.D$

y = B'C' + B'D' + AC' + AD

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

$A \overline{A} B \overline{B} C \overline{C} D \overline{D}$



www.  
32x8  
.com


$A \overline{A} B \overline{B} C \overline{C} D \overline{D}$

www.  
32x8  
.com

Truth Table

	A	B	C	D	Y
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	x
6	0	1	1	0	0
7	0	1	1	1	x
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

$$y = B'C' + B'D' + AC' + AD$$

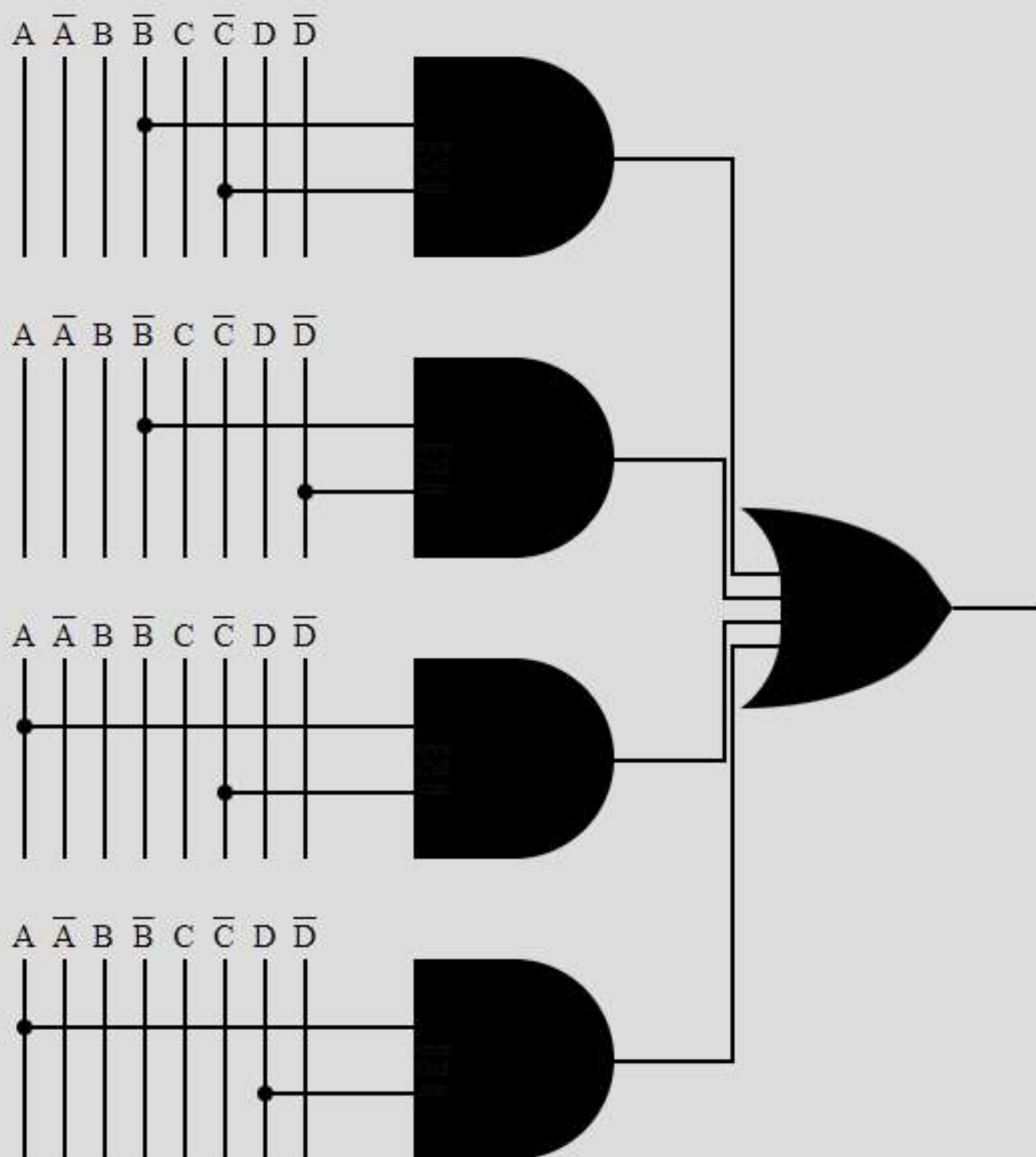

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	1	0	0	0
$\overline{A}.B$	0	1	1	0
$A.B$	1	1	0	0
$A.\overline{B}$	1	1	1	1

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(8,9,10,11)	$A.\overline{B}$
(8,9,12,13)	$A.\overline{C}$
(0,8)	$\overline{B}.\overline{C}.\overline{D}$
(5,7)	$\overline{A}.B.D$

$y = AB' + AC' + B'C'D' + A'BD$

$A \overline{A} B \overline{B} C \overline{C} D \overline{D}$

$A \overline{A} B \overline{B} C \overline{C} D \overline{D}$

$A \bar{A} B \bar{B} C \bar{C} D \bar{D}$



www.  
32x8  
.com


$A \bar{A} B \bar{B} C \bar{C} D \bar{D}$

www.  
32x8  
.com


Truth Table

	A	B	C	D	Y
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

$$y = AB'CD'$$

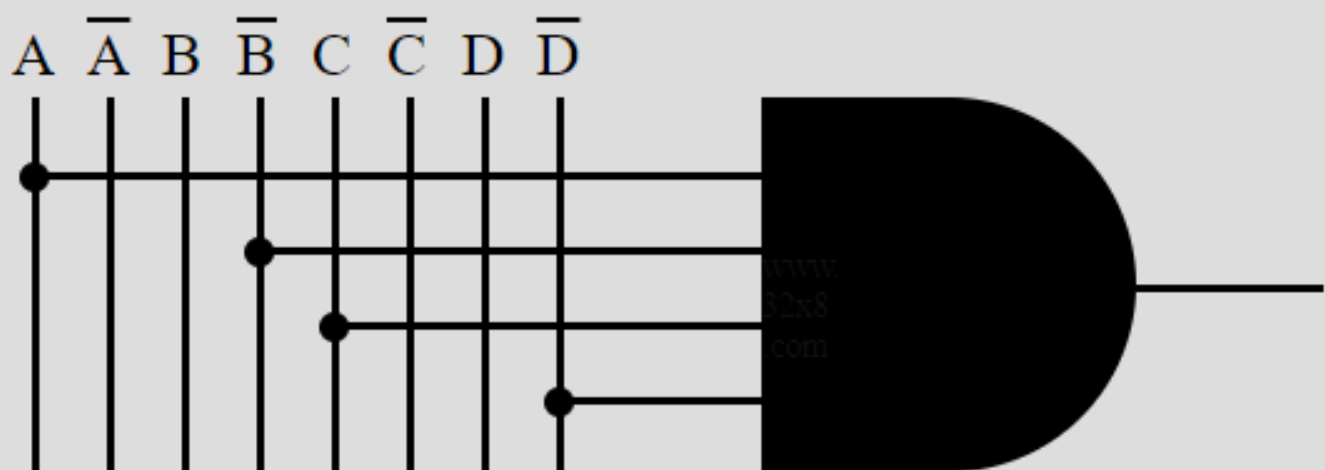

$y = AB' + A'BD$

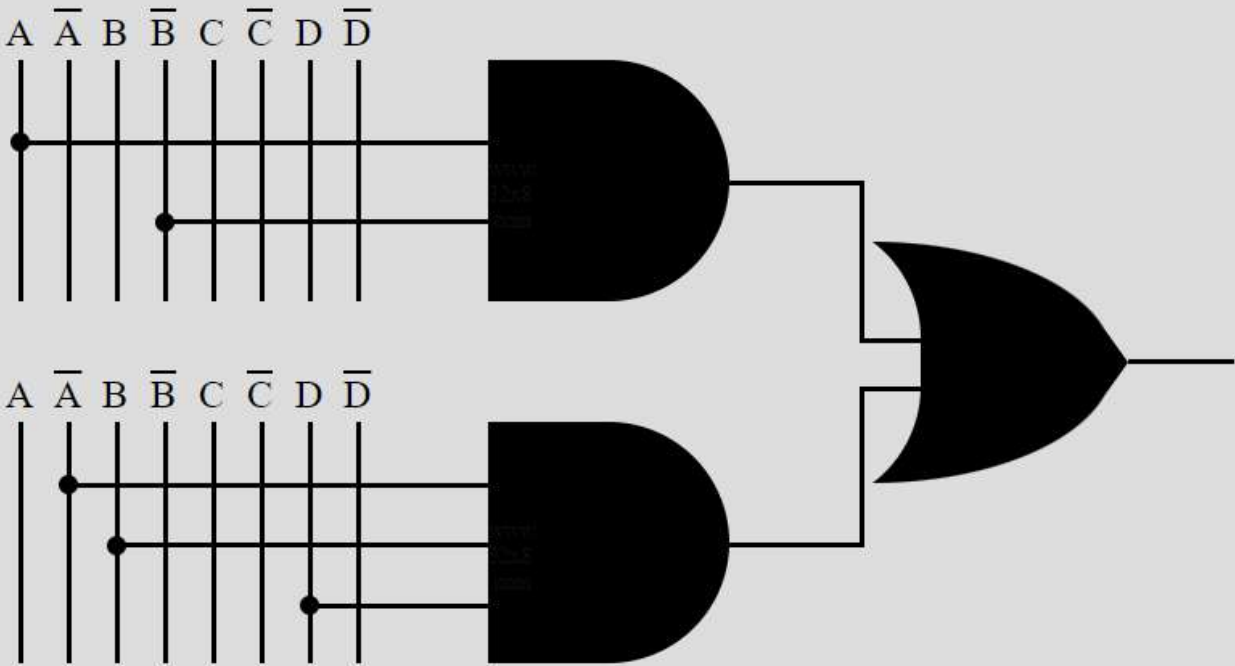

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	1	1	0	1
$\overline{A}.B$	0	1	x	0
$A.B$	1	1	1	0
$A.\overline{B}$	1	1	1	1

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(0,2,8,10)	$\overline{B}.\overline{D}$
(1,5,9,13)	$\overline{C}.D$
(8,9,12,13)	$A.\overline{C}$
(9,11,13,15)	$A.D$

y = B'D' + C'D + AC' + AD

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$



A A̅ B B̅ C C̅ D D̅



www.  
32x8  
.com


A A̅ B B̅ C C̅ D D̅

www.  
32x8  
.com

Truth Table

	A	B	C	D	Y
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	x
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

$$y = B'D' + C'D + AC' + AD$$

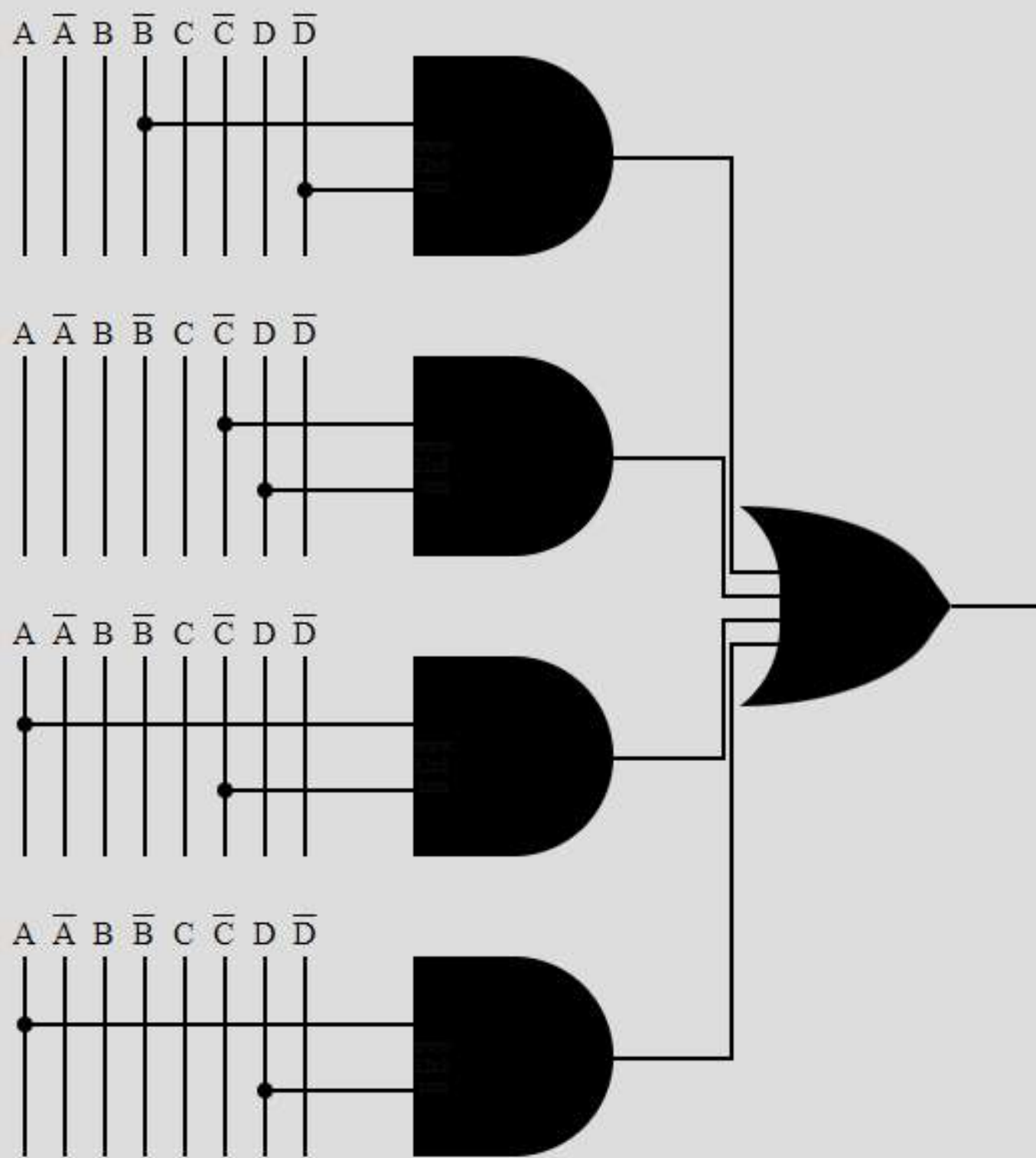

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	0	0	0
$\overline{A}.B$	0	1	x	0
$A.B$	x	1	0	0
$A.\overline{B}$	0	0	0	x

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(5,13)	$B.\overline{C}.D$
--------	--------------------

y = BC'D

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

Truth Table

	A	B	C	D	Y
0	0	0	0	0	x

1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	x
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	x
11	1	0	1	1	0
12	1	1	0	0	x
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022

SUM of PRODUCTS

Map

	$\overline{C}.\overline{D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	0	0	0
$\overline{A}.B$	0	0	0	0
$A.\overline{B}$	x	x	0	0
$A.B$	0	x	0	1

Map Layout

	$\overline{C}.\overline{D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.\overline{B}$	12	13	15	14
$A.B$	8	9	11	10

Groups

(10)	$A.\overline{B}.C.\overline{D}$
------	---------------------------------

y = AB'CD'

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

Truth Table

	A	B	C	D	Y
0	0	0	0	0	x

1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	x
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022

www.32x8.com

**SUM of PRODUCTS****Map**

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	1	0	0	0
$\overline{A}.B$	0	0	0	0
$A.B$	1	1	0	0
$A.\overline{B}$	0	1	1	0

**Map Layout**

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

**Groups**

(9,11)	$A.\overline{B}.D$
(12,13)	$A.B.\overline{C}$
(0)	$\overline{A}.\overline{B}.\overline{C}.\overline{D}$

$$y = AB'D + ABC' + A'B'C'D'$$

$$A \overline{A} B \overline{B} C \overline{C} D \overline{D}$$

www.  
32x8  
.com

$$A \overline{A} B \overline{B} C \overline{C} D \overline{D}$$

www.  
32x8  
.com

$A \bar{A} B \bar{B} C \bar{C} D \bar{D}$ 

www.  
32x8  
.com


**Truth Table**

	A	B	C	D	Y
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022



$$y = AC' + AB'D'$$

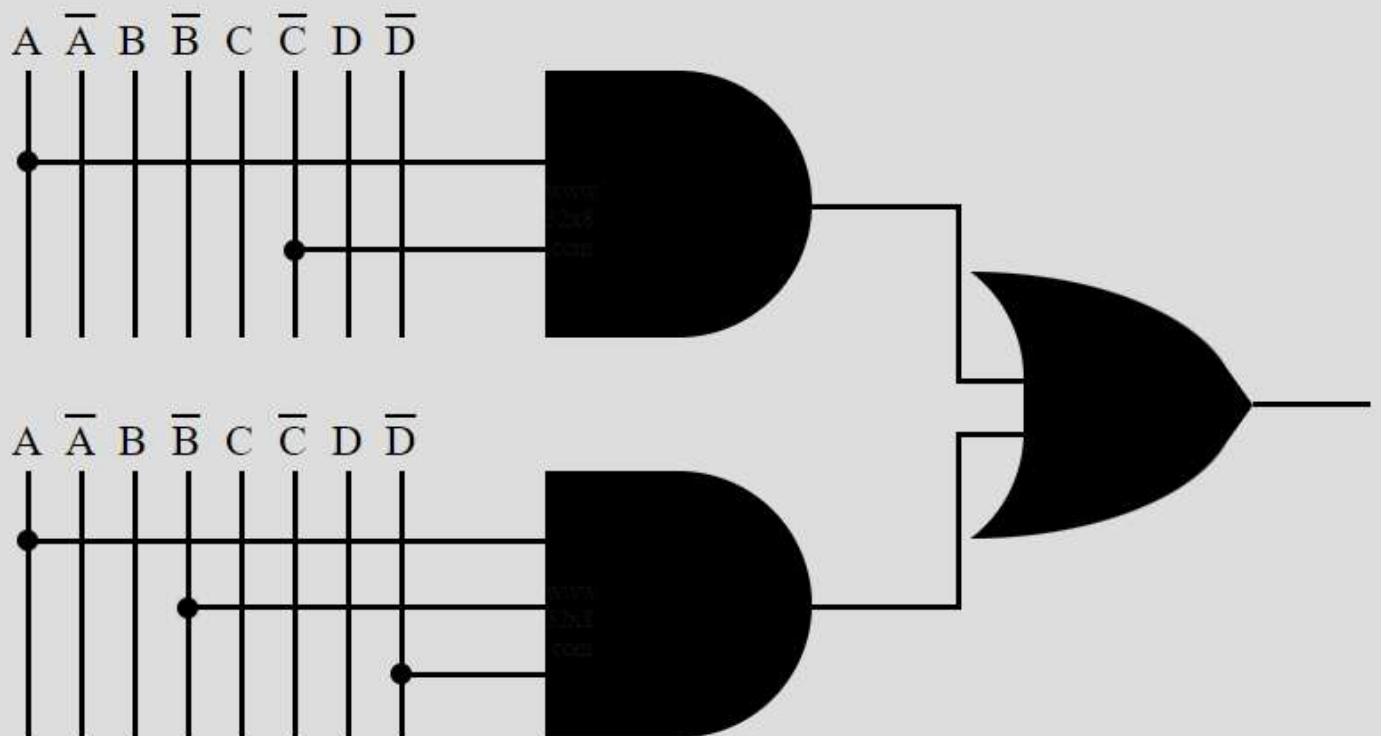

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	0	0	0
$\overline{A}.B$	0	0	0	0
$A.B$	x	x	0	0
$A.\overline{B}$	x	1	0	1

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(8,9,12,13)	$A.\overline{C}$
(8,10)	$A.\overline{B}.\overline{D}$

y = AC' + AB'D'

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$




**Truth Table**

	A	B	C	D	Y
0	0	0	0	0	x
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	x
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022

$$y = AC' + AB'D'$$

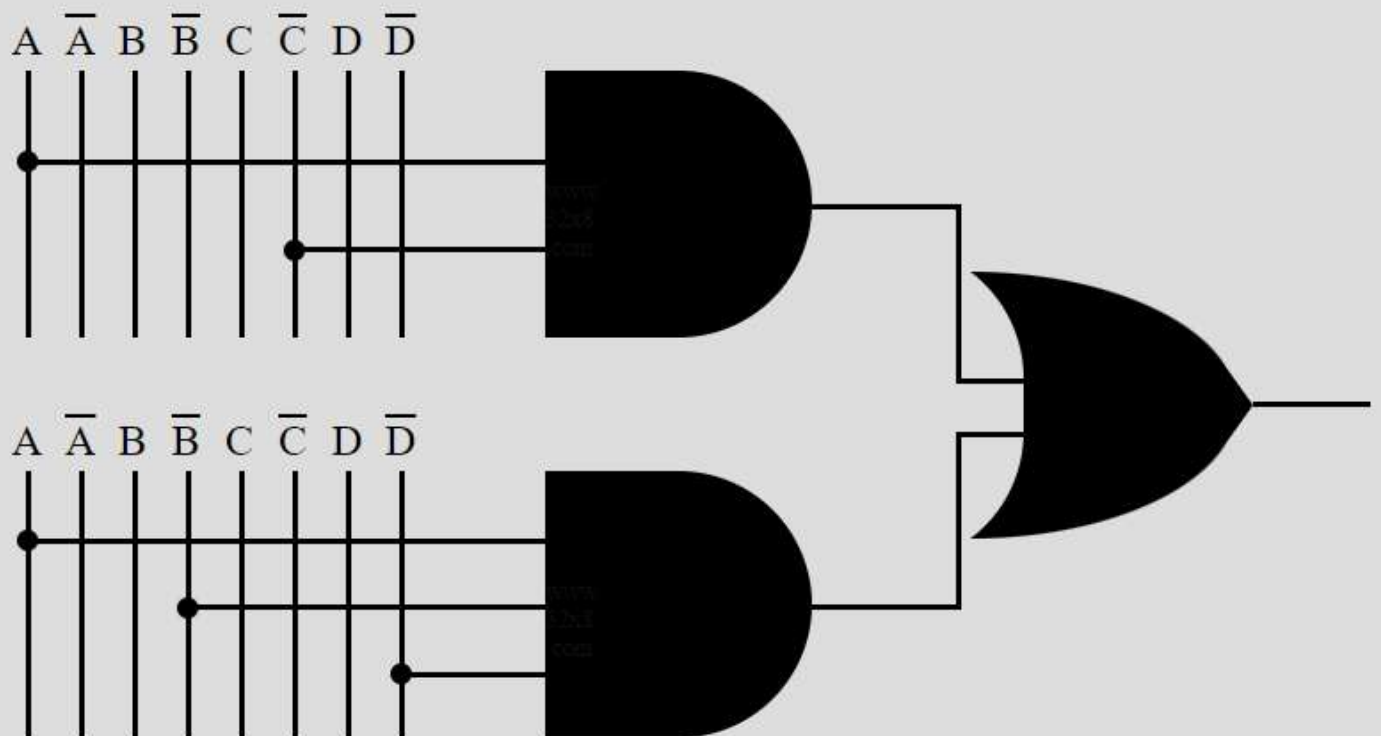

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A.B}$	x	0	0	0
$\overline{A}.B$	0	1	1	0
$A.B$	x	x	0	0
$A.\overline{B}$	x	1	1	1

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A.B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(8,9,10,11)	$A.\overline{B}$
(5,7)	$\overline{A}.B.D$

y = AB' + A'BD

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

www.  
32x8  
.com

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$



www.  
32x8  
.com

**Truth Table**

	A	B	C	D	Y
0	0	0	0	0	x
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	x
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022

www.32x8.com

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	x	0	x
$\overline{A}.B$	0	0	0	0
$A.\overline{B}$	1	1	x	0
$A.B$	x	x	x	x

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.\overline{B}$	12	13	15	14
$A.B$	8	9	11	10

Groups

(8,9,12,13)	$A.\overline{C}$
-------------	------------------

y = AC'

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

www.  
32x8  
.com

Truth Table


	A	B	C	D	Y
0	0	0	0	0	x

1	0	0	0	1	x
2	0	0	1	0	x
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	x
9	1	0	0	1	x
10	1	0	1	0	x
11	1	0	1	1	x
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	x

© 2014-2022



$$y = AC'$$

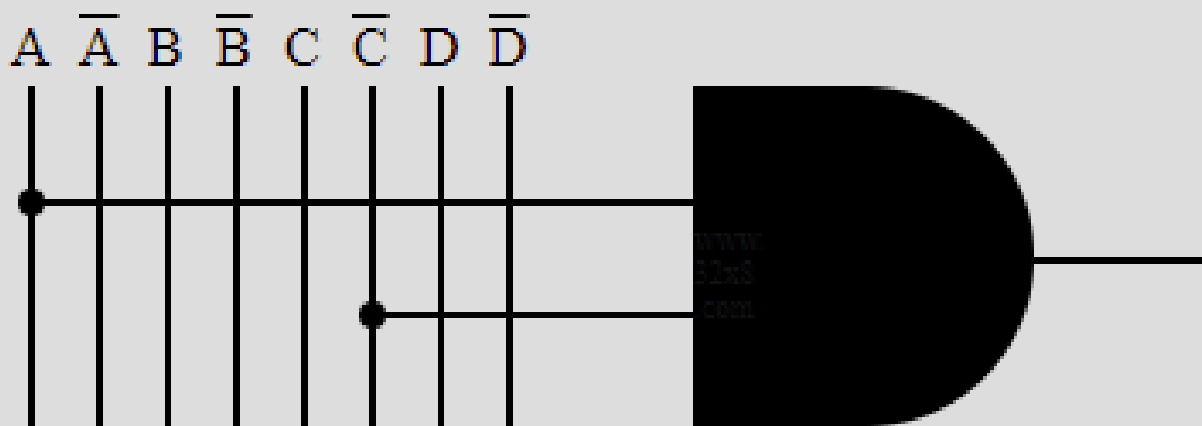

www.32x8.com

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	x	0	x
$\overline{A}.B$	0	0	x	0
$A.\overline{B}$	x	0	x	0
$A.B$	x	x	x	x

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.\overline{B}$	12	13	15	14
$A.B$	8	9	11	10

Groups

y = 0

Truth Table

	A	B	C	D	Y
0	0	0	0	0	x
1	0	0	0	1	x
2	0	0	1	0	x
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	x

8	1	0	0	0	x
9	1	0	0	1	x
10	1	0	1	0	x
11	1	0	1	1	x
12	1	1	0	0	x
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	x

© 2014-2022

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	x	0	x
$\overline{A}.B$	0	0	0	0
$A.B$	1	x	x	0
$A.\overline{B}$	x	x	x	x

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(8,9,12,13)	$A.\overline{C}$
-------------	------------------

y = AC'

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$


Truth Table

	A	B	C	D	Y
0	0	0	0	0	x

1	0	0	0	1	x
2	0	0	1	0	x
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	x
9	1	0	0	1	x
10	1	0	1	0	x
11	1	0	1	1	x
12	1	1	0	0	1
13	1	1	0	1	x
14	1	1	1	0	0
15	1	1	1	1	x

© 2014-2022

$$y = AC'$$

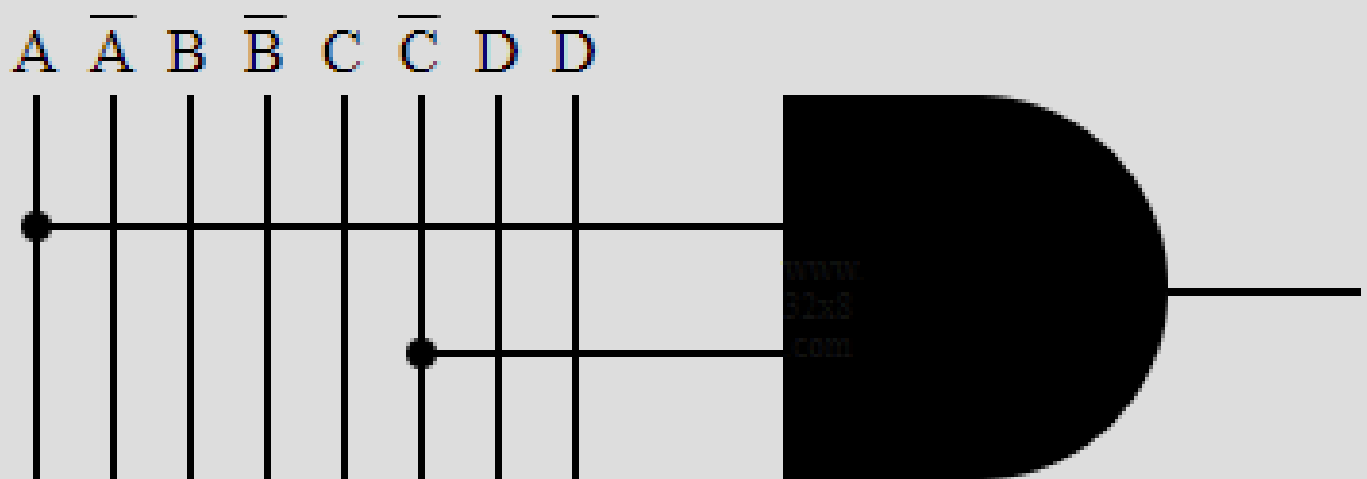

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	0	0	0
$\overline{A}.B$	0	1	1	0
$A.B$	x	x	0	0
$A.\overline{B}$	x	0	x	0

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.B$	12	13	15	14
$A.\overline{B}$	8	9	11	10

Groups

(5,7)	$\overline{A}.B.D$
-------	--------------------

y = A'BD

A  $\overline{A}$  B  $\overline{B}$  C  $\overline{C}$  D  $\overline{D}$

Truth Table


	A	B	C	D	Y
0	0	0	0	0	x

1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	x
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	x
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022



$$y = A'BD$$

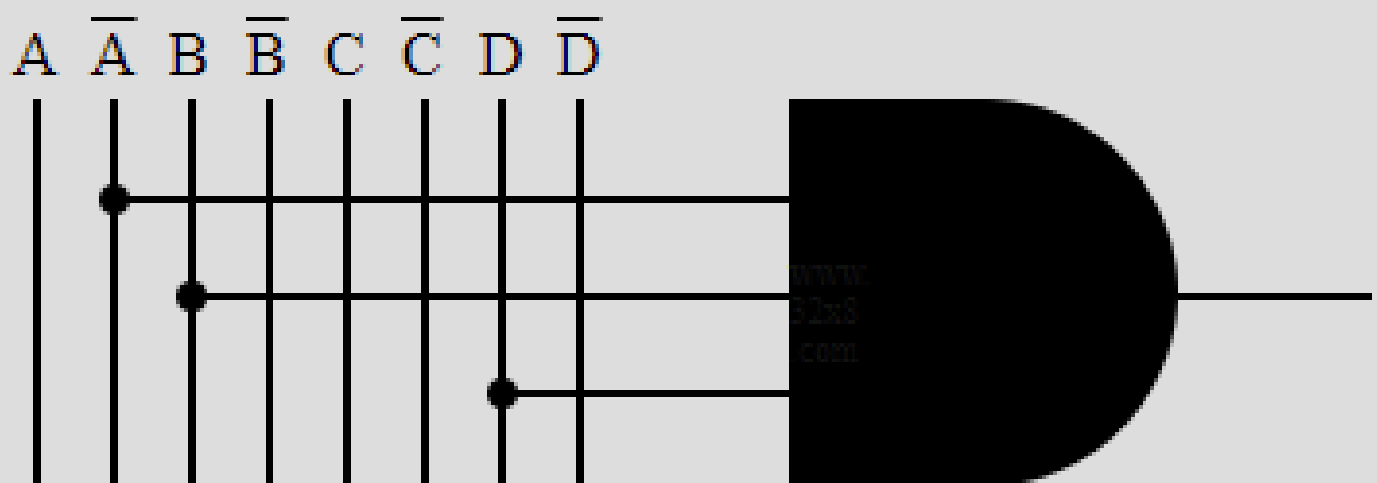

SUM of PRODUCTS

Map

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	x	0	0	0
$\overline{A}.B$	0	0	0	0
$A.\overline{B}$	0	x	0	0
$A.B$	x	0	x	0

Map Layout

	$\overline{C.D}$	$\overline{C}.D$	$C.D$	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.\overline{B}$	12	13	15	14
$A.B$	8	9	11	10

Groups

y = 0

Truth Table

	A	B	C	D	Y
0	0	0	0	0	x
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0

8	1	0	0	0	x
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	x
12	1	1	0	0	0
13	1	1	0	1	x
14	1	1	1	0	0
15	1	1	1	1	0

© 2014-2022

SUM of PRODUCTS

Map

	$\overline{C}. \overline{D}$	$\overline{C}.D$	$C.D$	$C. \overline{D}$
$\overline{A}.\overline{B}$	x	x	x	x
$\overline{A}.B$	x	x	x	x
$A.\overline{B}$	x	x	x	x
$A.B$	x	x	x	x

Map Layout

	$\overline{C}. \overline{D}$	$\overline{C}.D$	$C.D$	$C. \overline{D}$
$\overline{A}.\overline{B}$	0	1	3	2
$\overline{A}.B$	4	5	7	6
$A.\overline{B}$	12	13	15	14
$A.B$	8	9	11	10

Groups

$y = 0$   
 $y = 1$

Truth Table

	A	B	C	D	Y
0	0	0	0	0	x
1	0	0	0	1	x
2	0	0	1	0	x
3	0	0	1	1	x
4	0	1	0	0	x
5	0	1	0	1	x
6	0	1	1	0	x
7	0	1	1	1	x

8	1	0	0	0	x
9	1	0	0	1	x
10	1	0	1	0	x
11	1	0	1	1	x
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	x
15	1	1	1	1	x

© 2014-2022

Digital circuit and truth table of all control signals are separately given in a folder all\_ontroller\_ombined.pdf. Herewehaveshownalltogether.